

Student Names: Kübra Eryılmaz/ Ceren Dardağan

Student IDs:2014400186/ 2014400063


Session ID:2

Group ID:4

## CMPE 240 Experiment 5 Preliminary Work

**Step 1:** Design circuits with minimum number of components for each function of the ALU (This section should consist four circuits for each functionality of ALU) Show internal representation of each component as well. For example if you are using a full adder, draw inside of it as well. If you are using a component more than once, it is enough to draw inside of it once. You can represent repeated ones as black boxes providing their input/output labels clearly.

a)

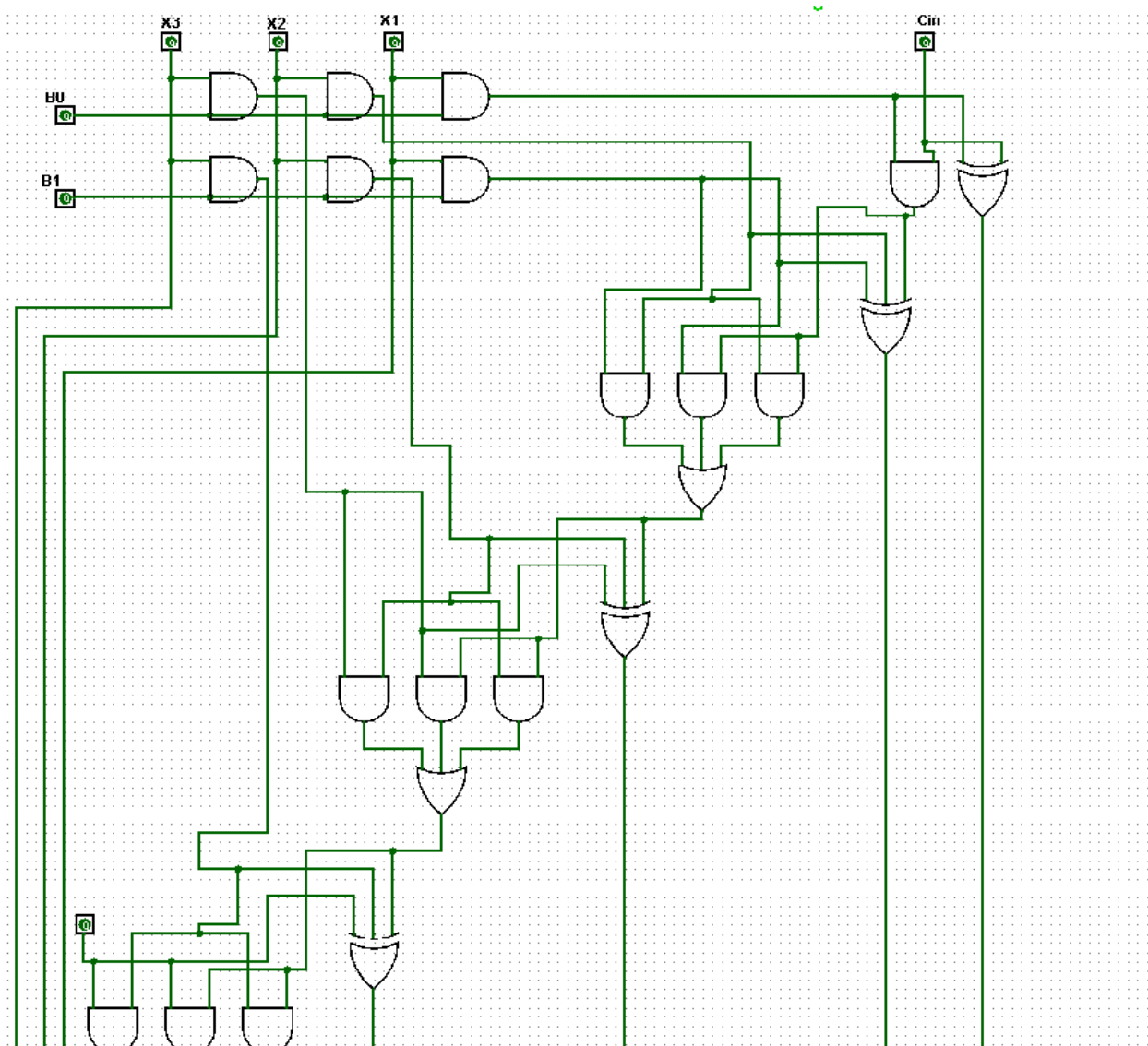


**Student Names: Kübra Eryılmaz/ Ceren Dardağan**

**Student IDs:2014400186/ 2014400063**

**Session ID:2**

**Group ID:4**

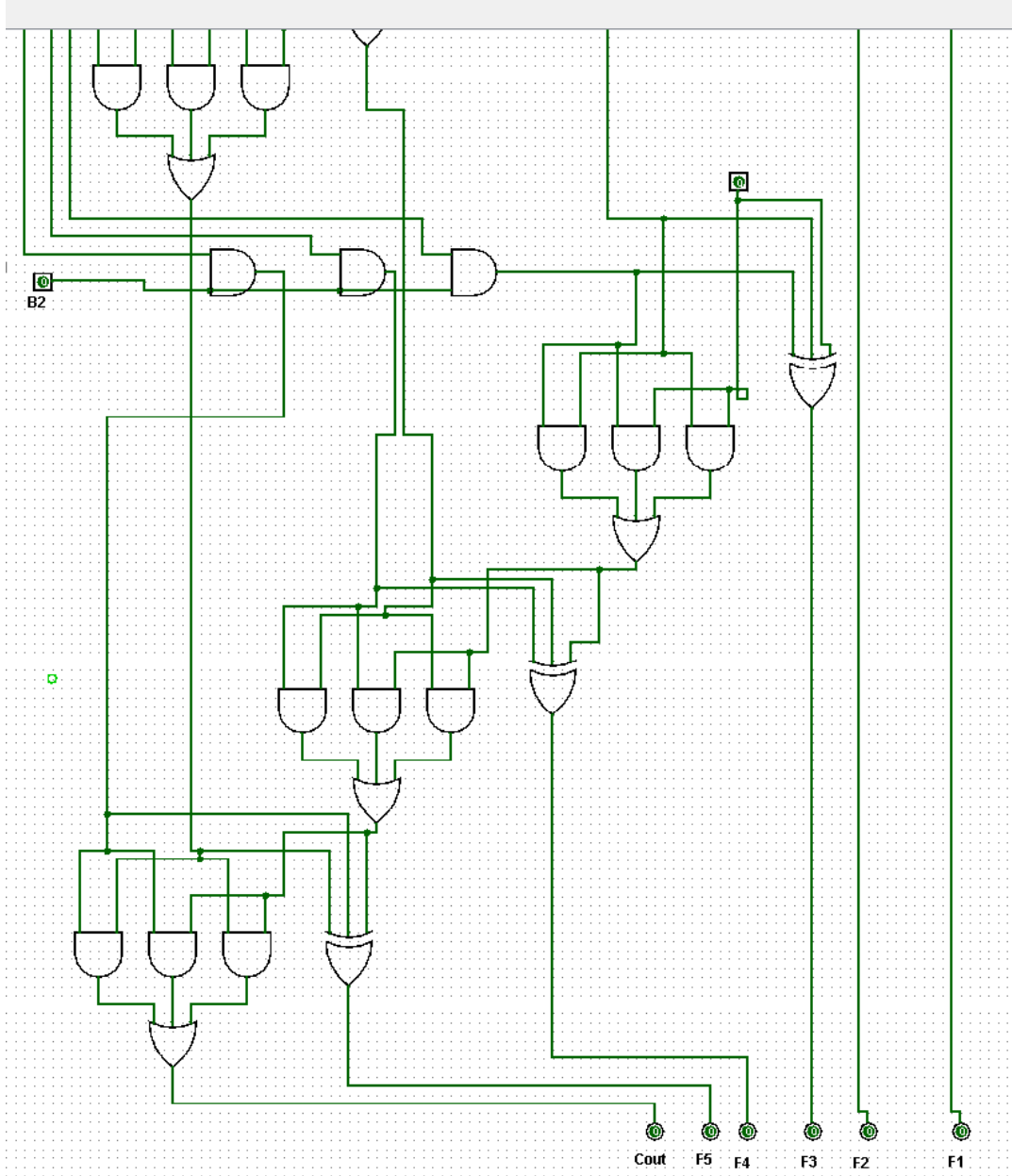


Student Names: Kübra Eryılmaz/ Ceren Dardağan

Student IDs:2014400186/ 2014400063


Session ID:2

Group ID:4

b)

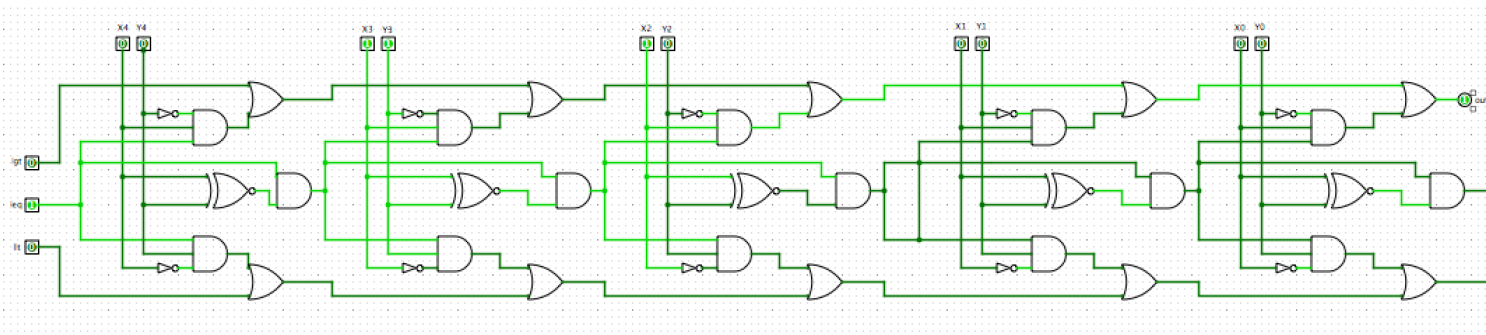

c)

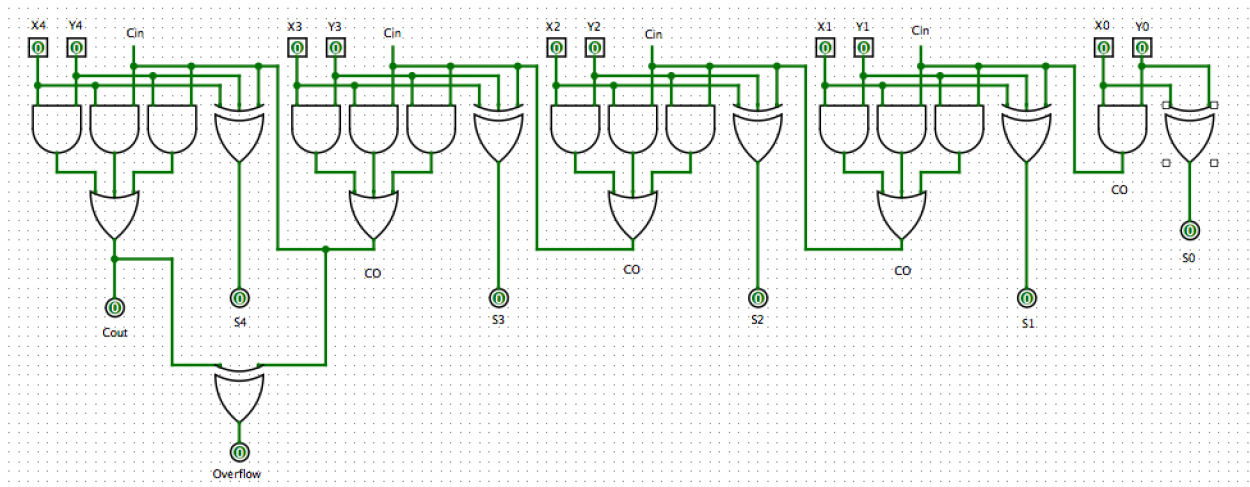


**Student Names: Kübra Eryılmaz/ Ceren Dardağan**

**Student IDs:2014400186/ 2014400063**

**Session ID:2**

**Group ID:4**

d)

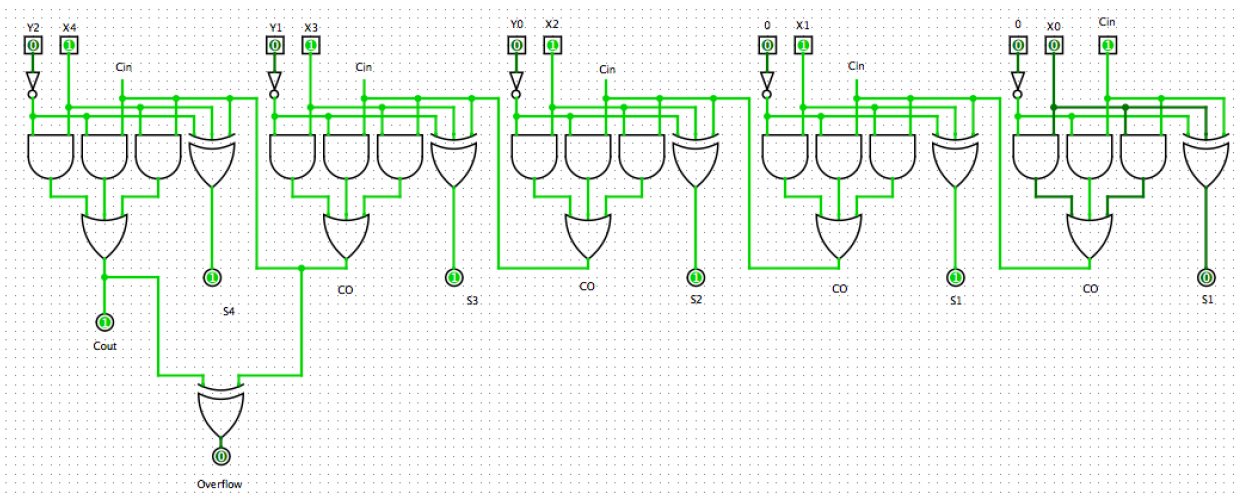

**Step 2: Merge all operations with select inputs and organize outputs, Try to minimize your implementation by using repetitions, draw final circuit as the minimized final design of the ALU.**

**Student Names: Kübra Eryılmaz/ Ceren Dardağan**

**Student IDs:2014400186/ 2014400063**

**Session ID:2**

**Group ID:4**

